

Q.7. A linear potentiometer of total variable length of 10cm, is to be designed for a resolution of 1.0 Ω /m. The maximum permissible non-linearity error value is desired as 2%. Consider the resistance of the voltage measuring device as 10K Ω . Compute the maximum and minimum value of the resistances with its corresponding error and resolution values. [5 Marks]