

Q5. Justify pros and cons of using large sized LUTs inside FPGAs. For example, to implement a 9 input function, would you prefer to have a 9-input LUT or go with multiple 3 input LUTs. [3]