

Q3. A designer wants to implement a 5-bit comparator using the carry logic of XC4000. A simplified block of a CLB is shown in the figure, using one or more such blocks, show how a 6 bit comparator can be built. Also show the circuit diagram of the logic implemented by the LUTs.
[6]

