

Q.2. Design a suitable bidirectional DC-DC converter for 10kW system with an output current of 75A and 80A during braking with a current and voltage ripple of 10% and 8% respectively. Assume switch loss is 2V. Make suitable assumptions. [8 Marks]